

THE KAVERY ENGINEERING COLLEGE*(An Autonomous Institution)*

UG/PG DEGREE END SEMESTER THEORY EXAMINATIONS, APRIL/MAY 2026

Second Semester

Electrical and Electronics Engineering




EE3251 / UEET24201 - ELECTRIC CIRCUIT ANALYSIS

Regulations - 2021 & 2024

Duration : 3 Hrs


Maximum : 100 Marks

PART - A (ANSWER ALL QUESTIONS) (Marks 10*2=20)

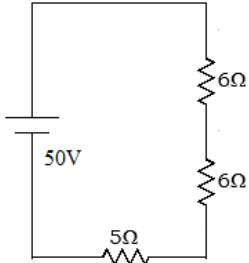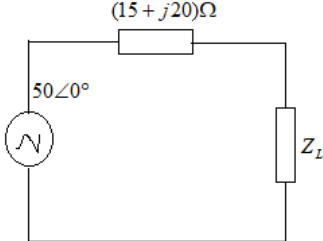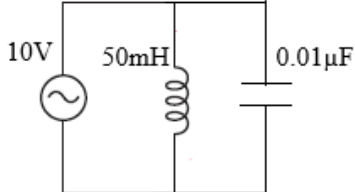
Q.No	Questions	BLT	CO	Marks
1.	Compute the voltage drop across the 3Ω resistor from the given circuit.	L3	1	2
				
2.	Sketch the impedance triangle of a simple RC circuit having $R=5\Omega$, $C=10\mu\text{F}$ and $V=10\sin 100\pi t$.	L3	1	2
3.	State. Norton's theorem	L1	2	2
4.	Find the value of load impedance for which the source delivers maximum power. Also calculate the value of maximum power.	L3	2	2
				
5.	Draw the equivalent circuit of a capacitor at $t = 0^+$ when i) there is no voltage at $t = 0^-$ ii) the capacitor is charged to V_0 .	L2	3	2
6.	Given that $i(t) = \frac{E}{R} e^{-\frac{t}{RC}}$, Compute $i(t)$ at one time constant.	L2	3	2
7.	Find the resonant frequency in the ideal parallel LC circuit.	L3	4	2
				
8.	Mention the significance of dot convention in coupled circuits.	L1	4	2
9.	In a balanced delta connected system, identify the values of I_L and V_L in terms of I_{ph} and V_{ph} .	L1	5	2
10.	Distinguish between balanced and unbalanced networks.	L1	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

Q.No	Questions	BLT	CO	Marks
11.	a i Determine the current through 5Ω resistor from the given circuit.	L3	1	8

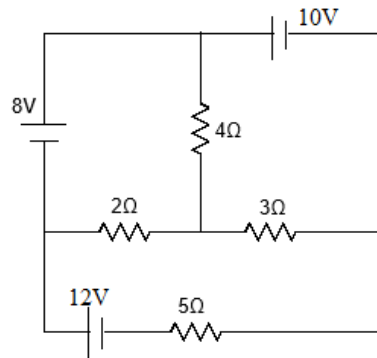


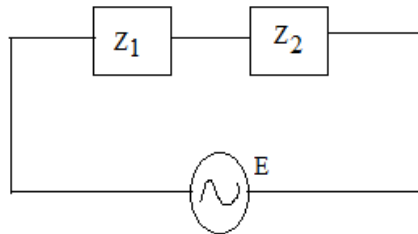- ii From the circuit shown, if $Z_1 = 5\angle 30^\circ$, $Z_2 = 4\angle 60^\circ$ and $E=100V$, calculate the current I and voltage drop across various impedances.




Or

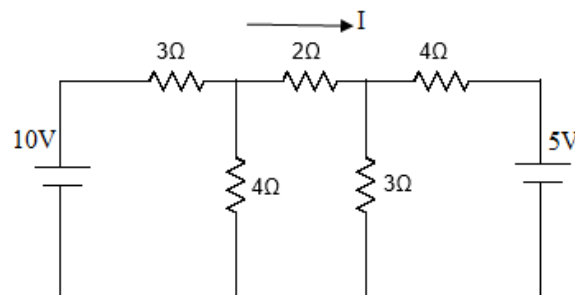
- b Using mesh analysis, find the current I flows through the circuit.



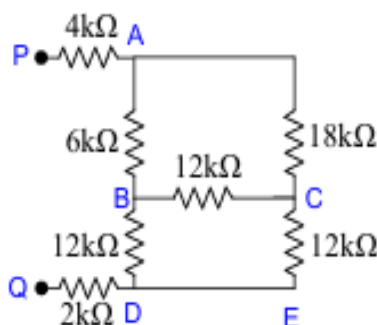12. a i Using star/delta transformation determine the resistance between A and B of the network shown.




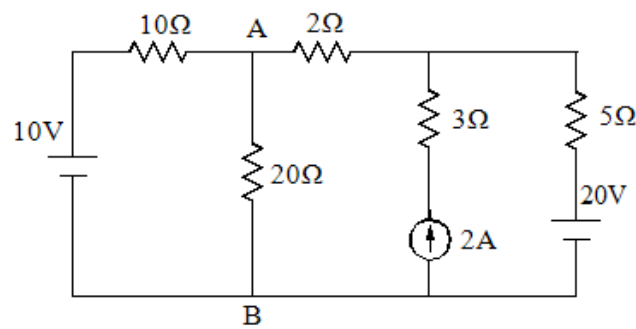- ii By using the superposition theorem, find the voltage across the 2Ω resistor from the given circuit. L3 2 8




Or

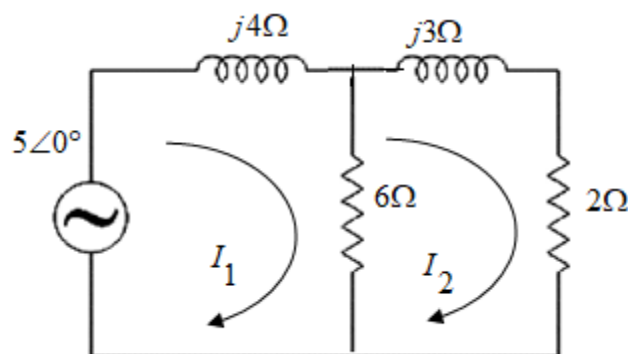
- b i For the circuit given, determine the currents by using mesh current equations. L3 2 8



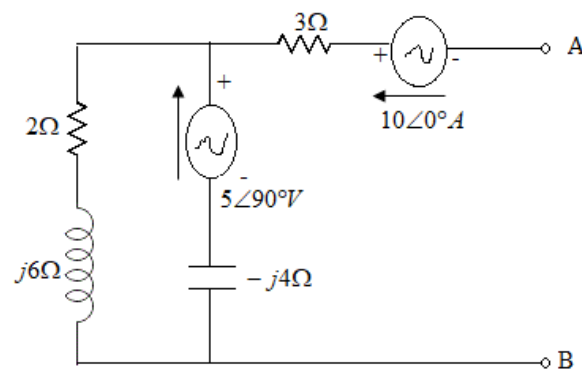- ii For the given circuit, determine the Thevenin's equivalent between the terminals AB. L3 2 8




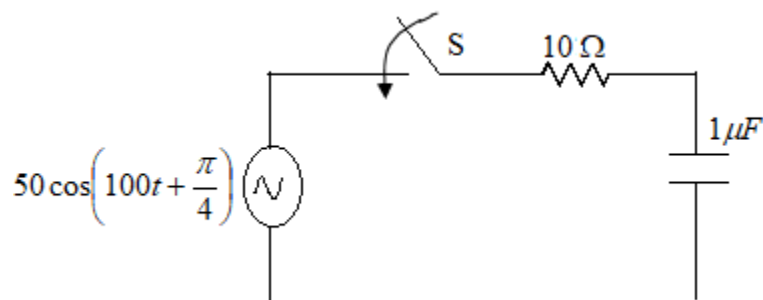13. a For the given circuit, analyze for the complete solution of current when switch S is closed at $t=0$. Applied voltage $e = 50\cos\left(100t + \frac{\pi}{4}\right)$. L4 3 16



Or

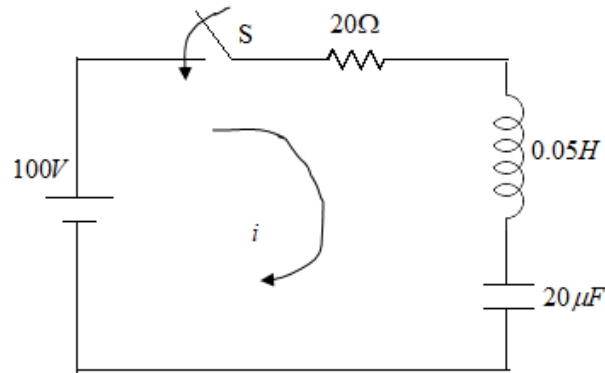- b For the given circuit, analyze the current transient when the switch is closed at $t=0$. L4 3 16



14. a i Derive an expression for half power frequencies of series resonant circuit. L2 4 8
- ii A series RLC Circuit with $R=10\Omega$, $L=1\text{mH}$ and $C=1\mu\text{F}$ has an applied voltage of 200V. Calculate i) resonant frequency ii) current at resonant frequency iii) impedance at 10Hz below resonant frequency. L3 4 8
- Or
- b i Two identical coupled coils are connected in series has an equivalent inductance values of 0.084H and 0.0354H. Find L_1 , L_2 and mutual inductance M . L3 4 8
- ii Derive the expression for coefficient of coupling between two coils. L2 4 8
15. a A balanced three phase star connected load with impedance $(8+j6)\Omega$ per phase is connected across a symmetrical 400V, 3 Φ , 50Hz supply. Determine the line currents and total power. L3 5 16
- Or
- b Demonstrate the power measurement in three phase circuits. Also brief about power factor calculations. L3 5 16