


THE KAVERY ENGINEERING COLLEGE*(An Autonomous Institution)***UG/PG DEGREE END SEMESTER THEORY EXAMINATIONS, APRIL/MAY 2026***Third Semester**Electrical and Electronics Engineering***UEET24301 - DIGITAL LOGIC CIRCUITS***Regulations - 2024**Duration : 3 Hrs**Maximum : 100 Marks***PART - A (ANSWER ALL QUESTIONS) (Marks 10*2=20)**

Q.No	Questions	BTL	CO	Marks																		
1.	Define Demorgan's Theorem.	L1	1	2																		
2.	Find the equivalent octal and decimal number for a given binary number 11010.	L1	1	2																		
3.	Draw a logic circuit for the truth table shown in figure.	L1	2	2																		
<table><tr><th colspan="2">Input</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>					Input		Output	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1
Input		Output																				
A	B	Y																				
0	0	1																				
0	1	0																				
1	0	0																				
1	1	1																				
4.	Compare between multiplexer and encoder.	L2	2	2																		
5.	Classify the different types of triggering signals used in synchronous sequential circuits.	L2	3	2																		
6.	Tell me the condition at which the two states are said to be equal.	L1	3	2																		
7.	Illustrate static 1 hazard with a neat waveform.	L2	4	2																		
8.	Recall the programmable logic devices.	L1	4	2																		
9.	Outline the different operators used in HDL.	L1	5	2																		
10.	Interpret the syntax of VHDL entity and architecture.	L2	5	2																		

PART - B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

<i>Q.No</i>	<i>Questions</i>	<i>BLT</i>	<i>CO</i>	<i>Marks</i>
11.	a Reduce the given Boolean expression using K-map and implement the reduced expression using AOI logic. $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$ Or b Reduce the given Boolean expression using Quine McCluskey method. $Y(a,b,c,d) = \sum m(0,1,4,5,13,14,15)$	L2	1	16
12.	a i Simplify a Full adder using two half adders with an OR gate.	L4	2	8
	ii Analysis the half subtractor using 2:4 decoder.	L4	2	8
	Or			
	b i Contrast the 1:4 Demultiplexer using logic gates.	L4	2	8
	ii Implement the given function using 8:1 multiplexer. $Y = \sum m(0,1,3,4,5,7,9,11,13,15)$	L4	2	8

 13. a i Construct the SR latch using NOR gates and explain its four mode of operation with its truth table. L3 3 8
- ii Organize the given state diagram using state reduction technique. L3 3 8



Or

- b Development of a synchronous counter to count 0,1,...,7 using JK Flip Flop. L3 3 16
14. a Design an asynchronous sequential circuit with two inputs x1 and x2 and one output Z. Initially, both inputs are equal to zero. When x1 or x2 becomes 1, the output Z becomes 1. When the second input also becomes 1, the output changes to 0. The output stays at 0 until the circuit goes back to the initial state. L4 4 16
- Or
- b i Implement the combinational circuit with a PLA having 3 inputs, 4 product terms and 2 outputs for the functions. $F1(A,B,C) = \sum (0, 1, 2, 4)$ $F2(A,B,C) = \sum (0, 5, 6, 7)$. L4 4 10
- ii Design a hazard free circuit for the given function $Y = \sum m(1,3,6,7)$. L4 4 6
15. a Construct the digital logic circuit to subtract three binary bits using logic gates and also develop the VHDL code for the same. L3 5 16
- Or
- b Apply an 8:1 multiplexer using basic logic gates and write the VHDL code for the developed model. L3 5 16