
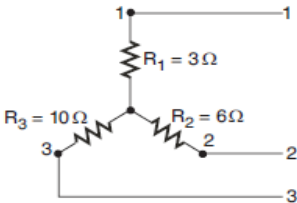


THE KAVERY ENGINEERING COLLEGE*(An Autonomous Institution)***B.E/B.TECH DEGREE END SEMESTER THEORY EXAMINATIONS, APRIL-MAY
2025****Second Semester****Electronics and Communication Engineering****EC3251 / UECT24201 - Circuit Analysis****Regulations – 2021/2024****Duration : 3 Hrs****Maximum : 100 Marks****PART – A (ANSWER ALL QUESTIONS) (Marks 10*2=20)**


Q.No	Questions	BL T	CO	Marks
1.	Define Kirchhoff's Voltage Law.	L1	1	2
2.	The equivalent resistance of two wires is $25\ \Omega$ when connected in series and $6\ \Omega$ when connected in parallel. Calculate the resistance of each wire.	L4	1	2
3.	What are the limitations of Super position theorem?	L1	2	2
4.	A star-connected network consists of three resistances $3\ \Omega$, $6\ \Omega$ and $10\ \Omega$. Convert the star-connected network into an equivalent delta-connected network.	L3	2	2
				
5.	A sinusoidal voltage is represented by the equation, $100 \sin(503t + 30^\circ)$ volts. What is the frequency and time period?	L2	3	2
6.	Write the expression for admittance of an RLC parallel circuit at half-power frequencies.	L1	3	2
7.	Determine the quality factor of an RLC series circuit with $R = 5\ \Omega$, $L = 0.01\text{H}$ and $C = 100\ \mu\text{F}$.	L2	4	2
8.	What is the time constant of an RL circuit with $R = 10\ \Omega$ and $L = 20\text{mH}$?	L1	4	2
9.	An ideal transformer has a turns ratio of 1:5. If the secondary voltage is 100 V, find the primary voltage.	L2	5	2
10.	State dot rule for coupled coils.	L1	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

Q.No	Questions	BL T	CO	Marks
11.	a i Obtain the current in each branch of the network shown in Fig. using Kirchhoff's Current Law.	L3	1	8

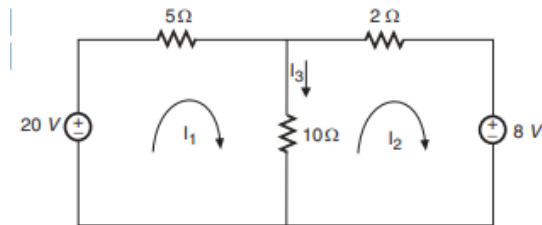


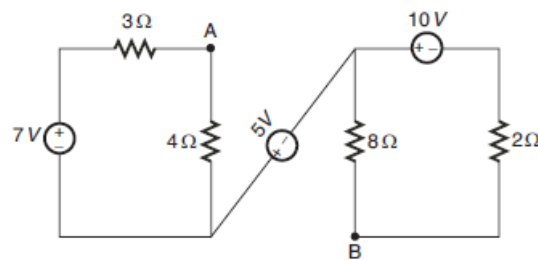- ii What is the voltage across A and B in the circuit shown in figure? L3 1 8




Or

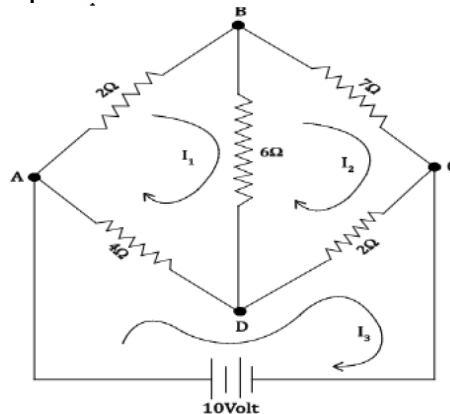- b The Wheat Stone Bridge Circuit as shown in Fig. Find Loop currents I_1 , I_2 , I_3 and also (i) Voltage across 6 Ohm Resistor (ii) Power Developed to 6 Ohm Resistor L3 1 16




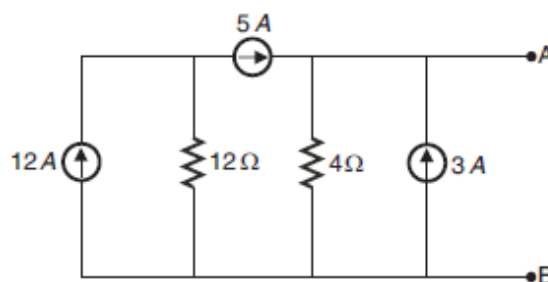12. a Determine Thevenin's and Norton's equivalents of the circuit shown in Fig. L3 2 16




Or

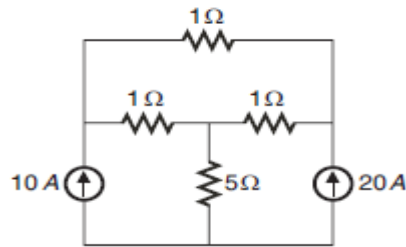
- b i Find the current through the 5 Ω resistor in the circuit shown in Figure using the superposition theorem. L3 2 8



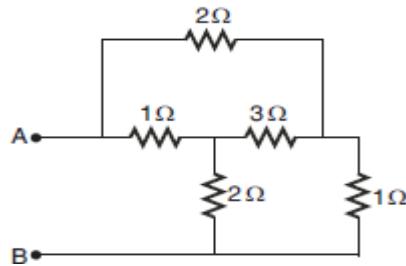
- ii Find the equivalent input resistance across terminals A and B of the bridged-T network shown in figure. L3 2 8



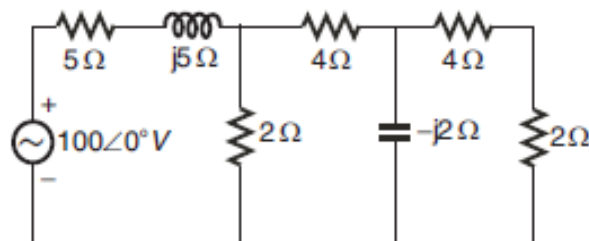13. a i A series combination of $12\ \Omega$ resistance and $600\ \mu\text{F}$ capacitance is connected to a 220 V, 50 Hz supply. Estimate the current, active power, reactive power and apparent power. Also estimate the voltage across R and C and draw the phasor diagram. L2 3 8
- ii Derive the phasor voltage-current relationships for resistor (R), inductor (L), and capacitor (C). L2 3 8
- Or**
- b Solve the currents in various branches of the circuit shown in Fig. by mesh analysis. L2 3 16



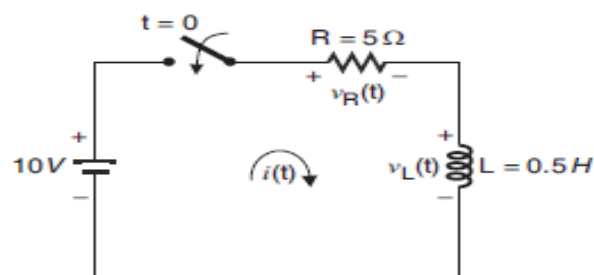14. a i In the RL circuit of Fig. the switch is closed at $t = 0$. Find the current $i(t)$ and the voltage across resistance and inductance. L2 4 10




- ii Derive the condition for resonance and the expression for resonant frequency in a series RLC circuit. L2 4 6

Or

- | | | | | | |
|---|----|--|----|---|---|
| b | i | Examine the transient response of RC circuit for unit step function. | L2 | 4 | 8 |
| | ii | Derive the admittance (Y) expression for a parallel RLC circuit and the resonant frequency (ignoring coil resistance). | L2 | 4 | 8 |

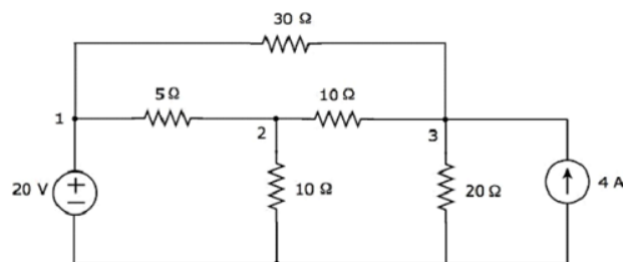15. a i An ideal transformer has a turns ratio of 1:5. If the secondary is connected to a $100\ \Omega$ load and the primary to a 10 V source, calculate:
- (i) Secondary voltage and current.
(ii) Power delivered to the load.
(iii) Reflected impedance at the primary

- ii Derive the relationship $l = b - n + 1$ (where l =loops, b =branches, n =nodes)
For a given circuit, calculate:
i. Number of links
ii. Number of independent loops



Or

- | | | | | | |
|---|----|---|----|---|---|
| b | i | A coil having an inductance of 100mH is magnetically coupled to another coil having an inductance of 900mH. The coefficient of coupling between the coils is 0.45. Calculate the equivalent inductance if the two coils are connected in a) series aiding, b) series opposing, c) parallel aiding and d) parallel opposing. | L4 | 5 | 8 |
| | ii | Determine the cut-set matrix and the current balance equation of the following graph. | L4 | 5 | 8 |

