

THE KAVERY ENGINEERING COLLEGE*(An Autonomous Institution)***UG/PG DEGREE END SEMESTER THEORY EXAMINATIONS, APRIL-MAY 2026****Second Semester****Applied Electronics****PAPT2421 - ANALOG AND MIXED SIGNAL IC DESIGN****Regulations - 2024****Duration: 3 Hrs.****Maximum: 100 Marks****PART – A(ANSWER ALL QUESTIONS) (Marks 10*2=20)**

Q.No	Questions	BLT	CO	Marks
1.	List two challenges in analog design?	L1	1	2
2.	Compare the common gate stage and cascade stage in terms of gain and input impedance?	L2	1	2
3.	Identify the key steps in the submicron CMOS process flow?	L1	2	2
4.	Describe the effect of circuit noise on operational amplifier performance?	L2	2	2
5.	Define differential non-linearity in a Digital-to-Analog Converter?	L1	3	2
6.	Differentiate between Flash ADC and Pipeline ADC architectures?	L2	3	2
7.	Identify the different MOS transistor layers used in layout design?	L1	4	2
8.	Discuss the importance of matching in analog layout techniques?	L2	4	2
9.	Name two types of voltage-controlled oscillators?	L1	5	2
10.	Describe the role of a charge pump in a PLL?	L2	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

Q.No	Questions	BLT	CO	Marks
11. a	Describe the structure and characteristics of MOSFETs?	L1	1	16
	Or			
b	Outline the different stages of a single-stage amplifier and their functions?	L1	1	16
12. a	Compare the different types of current mirrors used in analog circuit design?	L2	2	16
	Or			
b	Illustrate how circuit noise affects Op-Amp performance and discuss ways to mitigate it?	L2	2	16
13. a	Given a set of DAC specifications, determine the architecture that best suits the design requirements?	L3	3	16
	Or			
b	Analyse the impact of clock jitter on ADC performance and propose methods to improve it?	L3	3	16

14. a	Break down the different components of analog layout techniques and their significance in mixed-signal design?	L4	4	16
Or				
b	Examine the interconnection issues in mixed-signal layout and suggest possible design considerations to minimize them?	L4	4	16
15. a	Assess the non-ideal effects in PLLs and their impact on system performance?	L5	5	16
Or				
b	Justify the selection of a specific oscillator architecture for frequency synthesis applications based on performance metrics?	L5	5	16
